

# EECE 360: Systems and Control

## Midterm #1

Dr. Meeko Oishi

October 4, 2006

This midterm is closed-note, closed-book. A one-sided cheat-sheet is allowed. To get full credit, show all of your work.

### 1 Mass on a cart (50 points)

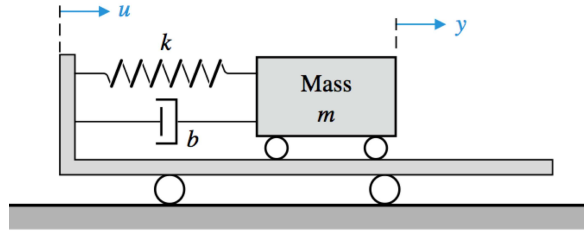


Figure 1: Mass  $m$  attached to a massless cart.

A mass as shown in Figure 1 sits on a massless cart. There is no friction between the cart and the ground, or between the mass and the cart. The output is the position of the mass, labeled  $y(t)$ , and the input is the position of the cart, labeled  $u(t)$ . The equations of motion for the mass  $m$  are:

$$m\ddot{y}(t) = -k(y(t) - u(t)) - b(\dot{y}(t) - \dot{u}(t)) \quad (1)$$

1. Find the transfer function  $G(s)$  with input  $u(t)$  and output  $y(t)$ .
2. Write the system in control canonical form. What are the matrices  $A, B, C, D$ ?
3. Find the state transition matrix  $\Phi(s)$  for general  $k, b, M$ . Now assume for the rest of the problem that  $k = 4$ ,  $b = 0$ , and  $M = 1$ . Rewrite  $\Phi(s)$  with these particular values.
4. What is the forced response in the  $s$ -domain for the input  $u(t) = \mathbf{1}(t)$ ? What is the forced response in the  $s$ -domain for the input  $u(t) = e^{-3t}$ ?
5. Given the initial condition  $x(0) = \begin{bmatrix} 1 & 1 \end{bmatrix}^T$ , what is the natural response in the  $s$ -domain? What is the natural response in the time-domain?

## 2 RLC Op-Amp Circuit (50 points)

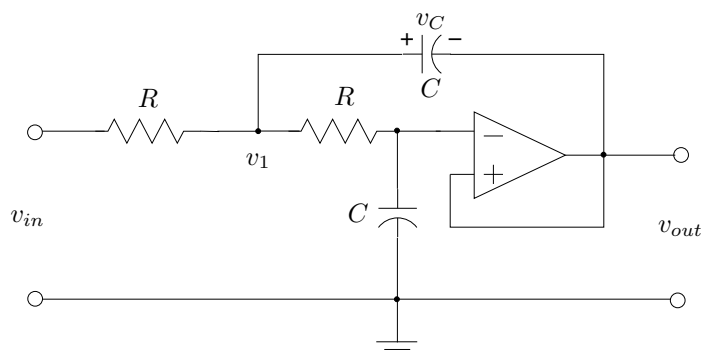


Figure 2: RLC op-amp circuit. Note that  $v_c = v_1 - v_{out}$ .

Consider the circuit shown in Figure 2.

1. Find the integro-differential equations which describe the circuit behavior. Write enough equations to be able to relate the output  $v_{out}$  to the input  $v_{in}$ .
2. Find the state-space representation using the state vector  $x = [v_{out}, v_C]$ , with input  $v_{in}$  and output  $v_0$ . Show that the state matrix is  $\begin{bmatrix} 0 & 1/(RC) \\ -1/(RC) & -2/(RC) \end{bmatrix}$ . What are  $B, C, D$ ?
3. Use these matrices to find the transfer function  $G(s)$  with input  $v_{in}$  and output  $v_C$ . (Only partial credit will be given if you find the transfer function in any other way, e.g. directly from Step 1).)
4. Show that the eigenvalues of  $A$  are equal to the poles of  $G(s)$ .
5. Multiple state-space representations exist for any given SISO system. Do multiple characteristic equations exist? Why or why not?