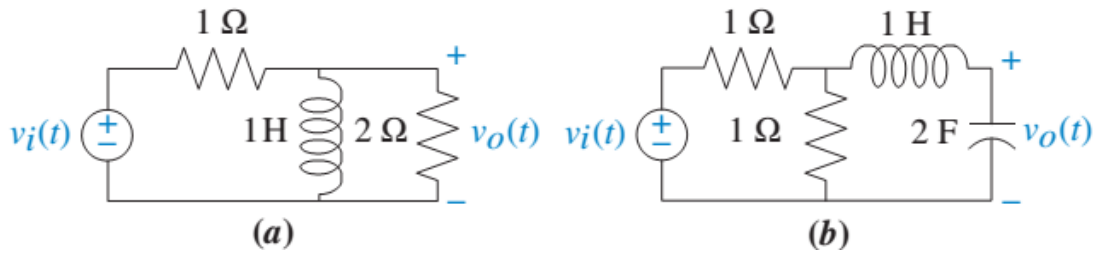


Assignment 4 (ELEC 341 L4_Model_ElecMech)

Problem 1:


Find the transfer function, $G(s) = V_o(s)/V_i(s)$ for each network shown in the following figure:



Solution:

problem 1

Assignment 4

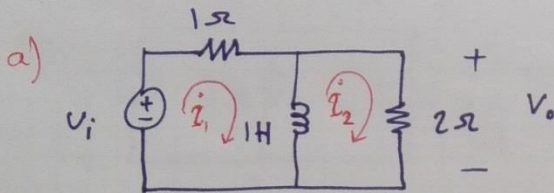

we have two methods for solving this problem: $\left\{ \begin{array}{l} \text{mesh analysis} \\ \text{node analysis} \end{array} \right.$
 this solution is with mesh analysis.

For writing the mesh equations, we can write them in time domain and then transfer them to Laplace or write them directly in Laplace domain. This solution is based on First method.

$$\text{KVL } ① : 1 \times i_1(t) + 1 \times \frac{d(i_1 - i_2)}{dt} = V_i(t)$$

$$\text{KVL } ② : 2 \times i_2(t) + 1 \times \frac{d(i_2 - i_1)}{dt} = 0$$

$$\xrightarrow{\text{Laplace}} \begin{cases} I_1(s) + s(I_1(s) - I_2(s)) = V_i(s) \\ 2I_2(s) + s(I_2(s) - I_1(s)) = 0 \end{cases} \quad \leftarrow \text{Note that initial condition } (i_{1,2}(0)) \text{ is zero because we want to calculate transfer function.}$$


$$\rightarrow \begin{cases} I_1(s+1) + I_2(-s) = V_i \\ I_1(-s) + I_2(2+s) = 0 \end{cases} \rightarrow \begin{bmatrix} s+1 & -s \\ -s & 2+s \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_i \\ 0 \end{bmatrix}$$

$$I_2 = \frac{\begin{vmatrix} s+1 & V_i \\ -s & 0 \end{vmatrix}}{(s+1)(s+2) - s^2} = \frac{s V_i}{s^2 + 2s + 2}$$

$$V_o = 2 I_2 = \frac{s}{1.5s+1} V_i \rightarrow \frac{V_o(s)}{V_i(s)} = \frac{s}{1.5s+1}$$

Assignment 4 (ELEC 341 L4_Model_ElecMech)

$$\frac{V_o(s)}{V_i(s)} = ?$$

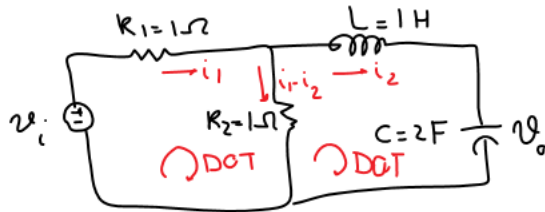

$$i_1 = i_2 + i_3 \rightarrow i_3 = i_1 - i_2$$

$$v_L = L \frac{di}{dt}; v_C = v_o = \frac{1}{C} \int_0^t i \cdot dt$$

$$R_1 i_1 + R_2 (i_1 - i_2) - v_i = 0 \quad i_1 + i_1 - i_2 - v_i = 0 \rightarrow 2i_1 - i_2 = v_i \xrightarrow{L}$$

$$L \frac{di_2}{dt} + \frac{1}{C} \int_0^t i_2 dt - R_2 (i_1 - i_2) = 0 \rightarrow 2I_1 - I_2 = V_i \quad (1)$$

$$\frac{di_2}{dt} + \frac{1}{2} \int_0^t i_2 dt - i_1 + i_2 = 0 \xrightarrow{L} sI_2 + \frac{1}{2s} I_2 - I_1 + I_2 = 0 \rightarrow$$

$$(s + \frac{0.5}{s}) I_2 + I_2 = I_1 \xrightarrow{\text{sub in (1)}} 2 \left\{ (s + \frac{0.5}{s}) I_2 + I_2 \right\} - I_2 = V_i \rightarrow$$

$$2 I_2 (s + \frac{0.5}{s}) + 2 I_2 - I_2 = V_i \rightarrow I_2 = \frac{s \cdot V_i}{2s^2 + s + 1} \xrightarrow{\text{sub in (1)}} 2I_1 - \frac{sV_i}{2s^2 + s + 1} = V_i \rightarrow$$


$$I_1 = \frac{V_i}{2} \left(\frac{2s^2 + 2s + 1}{2s^2 + s + 1} \right) \quad v_o = \frac{1}{2} \int_0^t i_2 dt \xrightarrow{L} V_o = \frac{I_2}{2s} \rightarrow V_o = \frac{1}{2s} \cdot \frac{sV_i}{2s^2 + s + 1}$$

$$\rightarrow \frac{V_o}{V_i} = \frac{1}{4s^2 + 2s + 2}$$

Assignment 4 (ELEC 341 L4_Model_ElecMech)

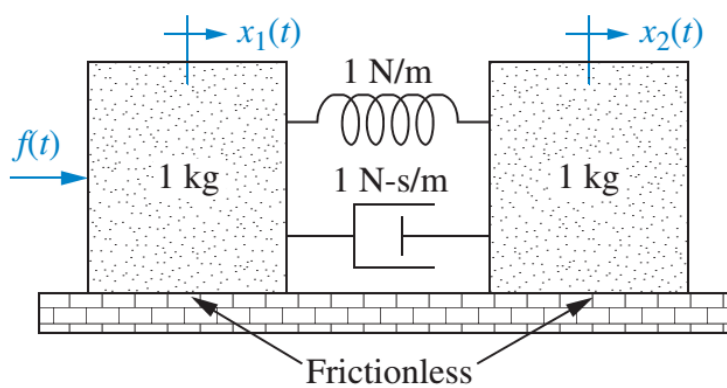
Problem 2:

Find the transfer function, $G(s) = X_2(s)/F(s)$, for the translational mechanical network shown in figure:



Assignment 4 (ELEC 341 L4_Model_ElecMech)

Solution:

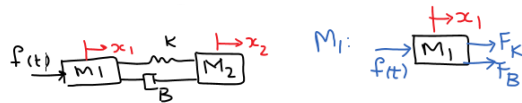

$$M_1 \ddot{x}_1 = F_K + F_B + f(t)$$

$$F_K \text{ is always: } F_K = -k(x_{\text{left}} - x_{\text{right}}) \Rightarrow$$

$$F_B \text{ " " : } F_B = -B(\dot{x}_{\text{left}} - \dot{x}_{\text{right}})$$

$$M_1 \ddot{x}_1 = -k(x_1 - x_2) - B(\dot{x}_1 - \dot{x}_2) + f(t) \rightarrow$$

$$M_1 \ddot{x}_1 = f(t) - B(\dot{x}_1 - \dot{x}_2) - K(x_1 - x_2)$$

$$M_2: \quad F_K \quad \xrightarrow{\dot{x}_2} \quad M_2 \quad \ddot{x}_2 = -F_K - F_B =$$

$$= -\{(-k)(x_1 - x_2) + (-B)(\dot{x}_1 - \dot{x}_2)\}$$

$$\rightarrow M_2 \ddot{x}_2 = -B(\dot{x}_2 - \dot{x}_1) - K(x_2 - x_1)$$

$$\rightarrow \begin{cases} \ddot{x}_1 = f(t) - \dot{x}_1 + \dot{x}_2 - x_1 + x_2 \\ \ddot{x}_2 = -\dot{x}_2 + \dot{x}_1 - (x_2 - x_1) \end{cases} \rightarrow \begin{cases} \ddot{x}_1 + \dot{x}_1 - \dot{x}_2 + x_1 - x_2 = f(t) \\ \ddot{x}_2 + \dot{x}_2 - \dot{x}_1 + x_2 - x_1 = 0 \end{cases}$$

$$\xrightarrow{\mathcal{L}} \begin{cases} s^2 X_1 + s X_1 - s X_2 + X_1 - X_2 = F(s) \\ s^2 X_2 + s X_2 - s X_1 + X_2 - X_1 = 0 \end{cases} \rightarrow$$


$$\begin{cases} (s^2 + s + 1) X_1 - (s + 1) X_2 = F(s) \\ -(s + 1) X_1 + (s^2 + s + 1) X_2 = 0 \end{cases} \rightarrow$$

$$X_2 = \frac{\begin{vmatrix} s^2 + s + 1 & F(s) \\ -(s + 1) & 0 \end{vmatrix}}{\begin{vmatrix} s^2 + s + 1 & -(s + 1) \\ -(s + 1) & s^2 + s + 1 \end{vmatrix}} = \frac{+F(s)(s + 1)}{(s^2 + s + 1)^2 - (s + 1)^2} \rightarrow$$

$$X_2 = \frac{(s + 1) F(s)}{s^2(s^2 + 2s + 2)} \rightarrow \boxed{\frac{X_2}{F(s)} = \frac{(s + 1)}{s^2(s^2 + 2s + 2)}}$$

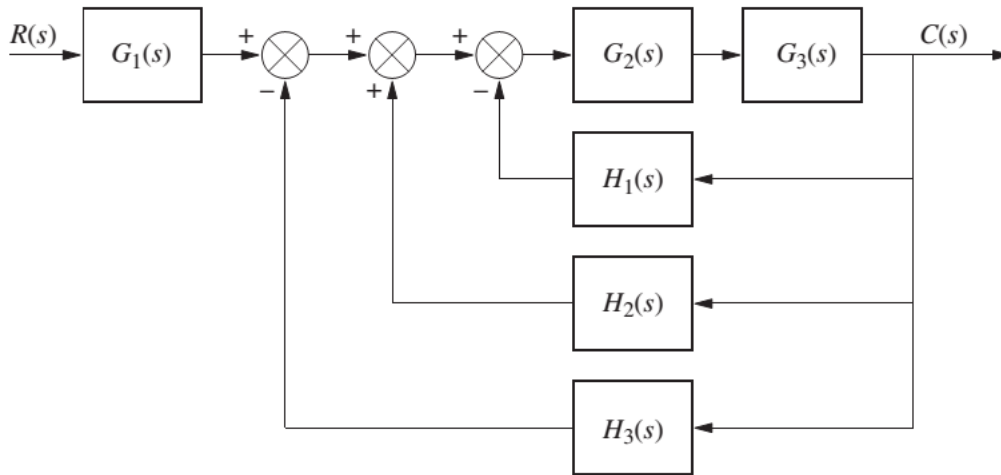Problem 3:

Reduce the block diagram shown in figure to a single transfer function:




Solution:

We solve the problem by following the steps in Figure . First, the three summing junctions can be collapsed into a single summing junction, as shown in Figure (a).


Second, recognize that the three feedback functions, $H_1(s)$, $H_2(s)$, and $H_3(s)$, are connected in parallel. They are fed from a common signal source, and their outputs are summed. The equivalent function is $H_1(s) - H_2(s) + H_3(s)$. Also recognize that $G_2(s)$ and $G_3(s)$ are connected in cascade. Thus, the equivalent transfer function is the product, $G_3(s)G_2(s)$. The results of these steps are shown in Figure (b).

Finally, the feedback system is reduced and multiplied by $G_1(s)$ to yield the equivalent transfer function shown in Figure (c).

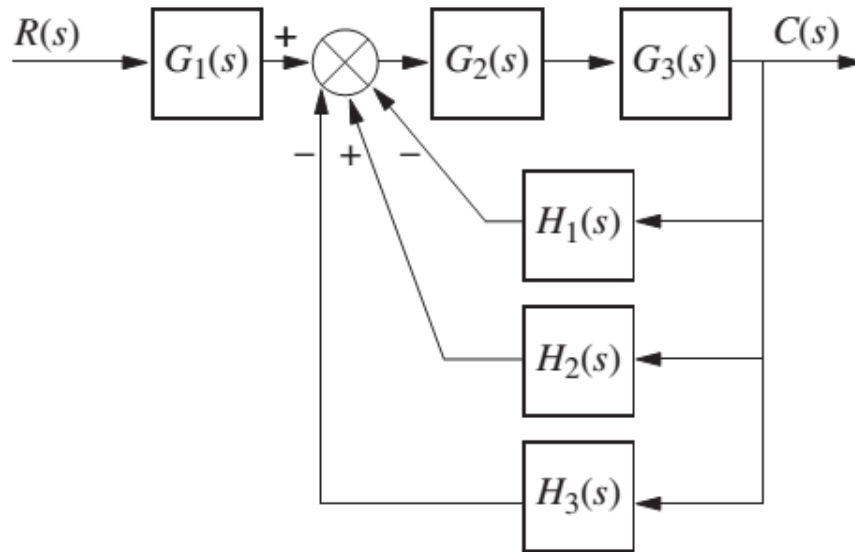
Assignment 4 (ELEC 341 L4_Model_ElecMech)



(a)

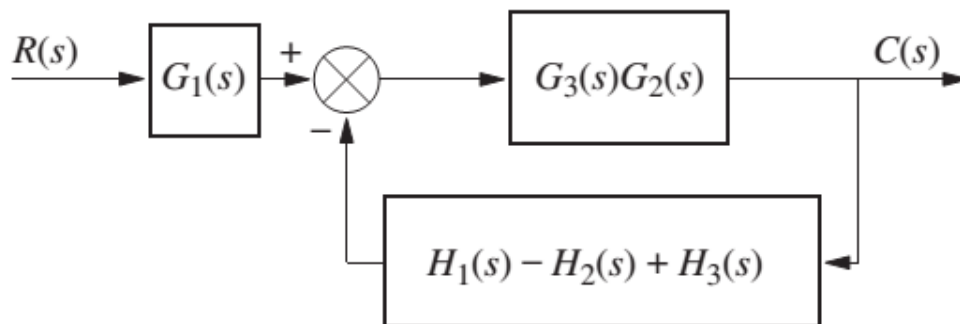

(b)

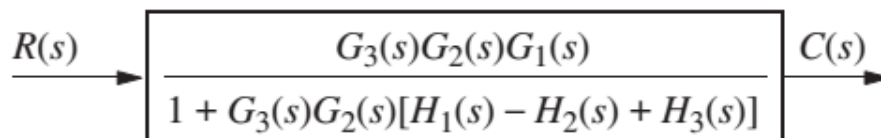

(c)

Assignment 4 (ELEC 341 L4_Model_ElecMech)

Problem 4:

Calculate the transfer function of the system represented in the state space model as

$$\dot{X} = \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} -1 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} [u]$$
$$Y = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

Solution:

$$\frac{Y(s)}{U(s)} = C(sI - A)^{-1}B + D$$

Here,

$$A = \begin{bmatrix} -1 & -1 \\ 1 & 0 \end{bmatrix}, \quad B = \begin{bmatrix} 1 \\ 0 \end{bmatrix}, \quad C = \begin{bmatrix} 0 & 1 \end{bmatrix} \quad \text{and} \quad D = [0]$$

The formula for the transfer function when $D = [0]$ is -

$$\frac{Y(s)}{U(s)} = C(sI - A)^{-1}B$$

Substitute, A, B & C matrices in the above equation.

$$\begin{aligned} \frac{Y(s)}{U(s)} &= \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} s+1 & 1 \\ -1 & s \end{bmatrix}^{-1} \begin{bmatrix} 1 \\ 0 \end{bmatrix} \\ \Rightarrow \frac{Y(s)}{U(s)} &= \begin{bmatrix} 0 & 1 \end{bmatrix} \frac{\begin{bmatrix} s & -1 \\ 1 & s+1 \end{bmatrix}}{(s+1)s - 1(-1)} \begin{bmatrix} 1 \\ 0 \end{bmatrix} \\ \Rightarrow \frac{Y(s)}{U(s)} &= \frac{\begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} s \\ 1 \end{bmatrix}}{s^2 + s + 1} = \frac{1}{s^2 + s + 1} \end{aligned}$$

Therefore, the transfer function of the system for the given state space model is

$$\frac{Y(s)}{U(s)} = \frac{1}{s^2 + s + 1}$$

Find $(sI-A)^{-1} = ?$

$$s \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \begin{bmatrix} -1 & -1 \\ 1 & 0 \end{bmatrix} = \begin{bmatrix} s & 0 \\ 0 & s \end{bmatrix} - \begin{bmatrix} -1 & -1 \\ 1 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} s & 0 \\ 0 & s \end{bmatrix} + \begin{bmatrix} 1 & 1 \\ -1 & 0 \end{bmatrix} \rightarrow sI-A = \begin{bmatrix} s+1 & 1 \\ -1 & s \end{bmatrix}$$

$$(sI-A)^{-1} = ? ; Q = \begin{bmatrix} a & b \\ c & d \end{bmatrix}^{-1} = \frac{1}{\det Q} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$


$$\det(sI-A) = s(s+1)+1 = s^2+s+1 \rightarrow$$

$$(sI-A)^{-1} = \frac{1}{s^2+s+1} \begin{bmatrix} s & -1 \\ 1 & s+1 \end{bmatrix}$$



Assignment 4 (ELEC 341 L4_Model_ElecMech)

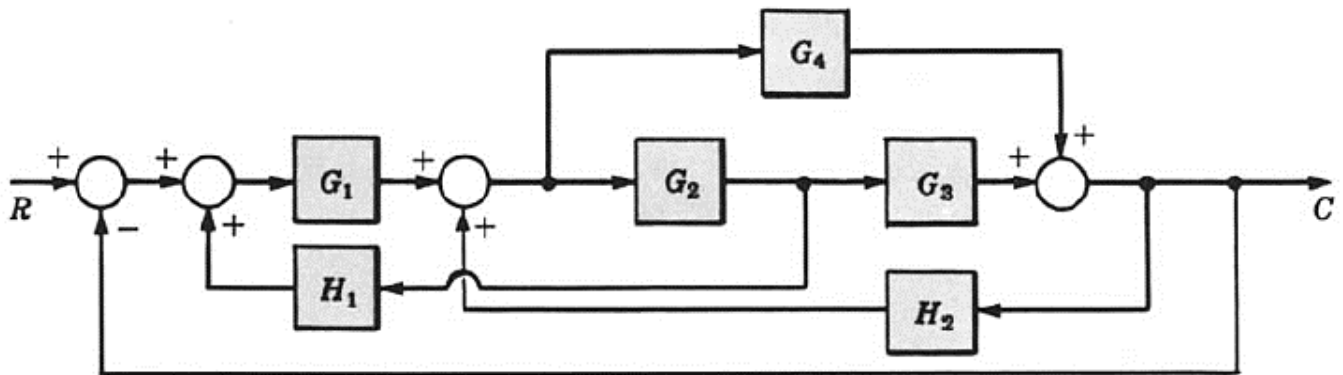Problem 5:

Find the signal flow graph for the following block diagram:



Solution:

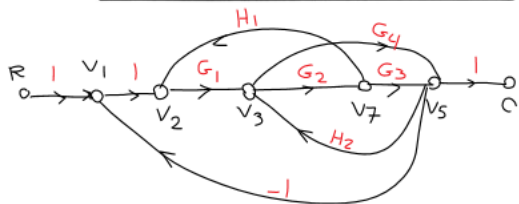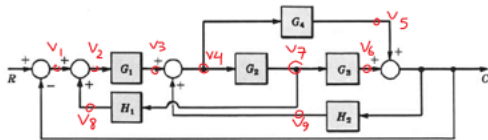

↓ simplify

